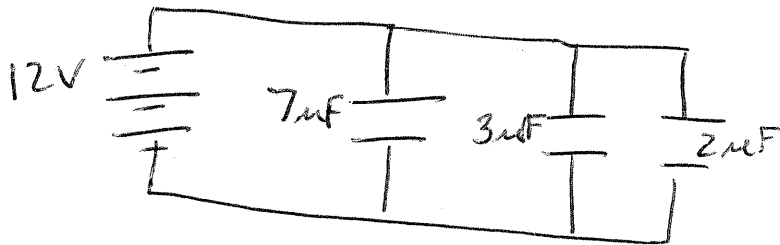


Name _____


Per. _____

AP 2
Hand Drawn Capacitor Circuits


① Find Q + V for each capacitor




②

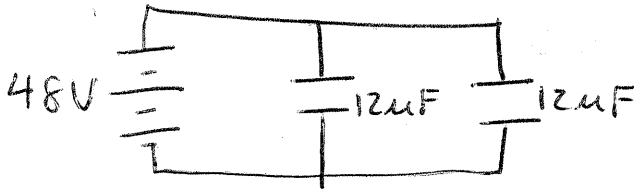


③

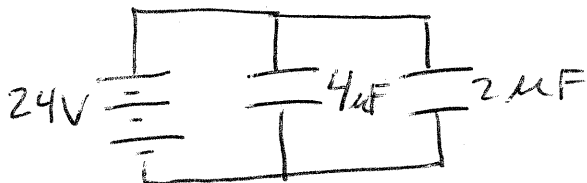

④

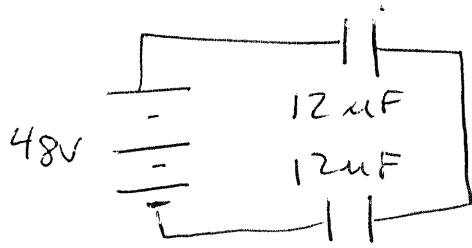

⑤

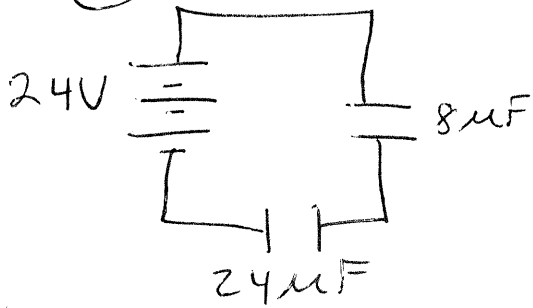

⑥

