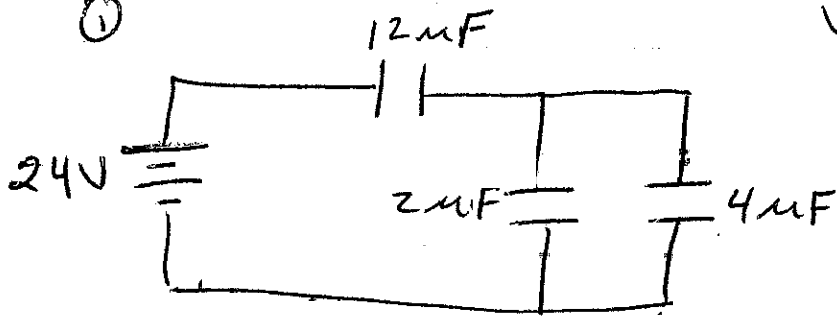


Name _____ Per. _____


Capacitors in Combination

Find C_{eq} , Q_0 and V/Q for each capacitor.


①



②

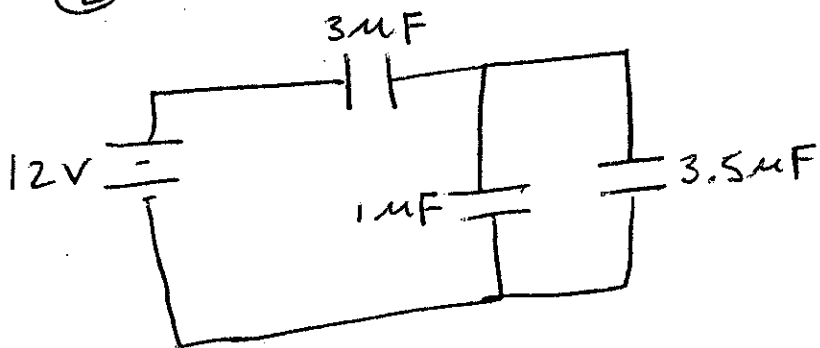

③

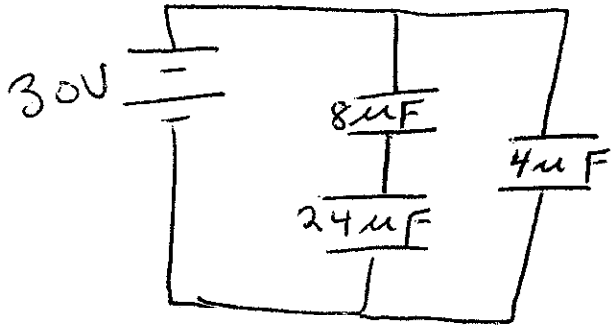

④

